

### QUESTION ONE 30 MARKS (COMPULSORY)

- a. By use of operator tables to form a truth table, prove the given Boolean equation

$$x \cdot (y + z) = (x \cdot y) + (x \cdot z)$$

4 Marks

- b. Solve

i.  $35_{10} - 72_{10}$  using two's complement format with 8-bit numbers.

3 Marks

ii.  $65_{10} - 25_{10}$  using one's complement format with 8-bit numbers.

3 Marks

- c. Design and implement a circuit that counts the number of 1's present in 3 inputs A, B and C. Its output is a two-bit number  $X_1X_0$ , representing that count in binary. Using a K-map, find the minimized logic equations for outputs  $X_1$  and  $X_0$ . Assume active-HIGH logic.

7 Marks

3 Marks

- d. Simplify the given Boolean equation

$$(\overline{A} \overline{B} \overline{C}) + (\overline{A} \overline{B} C)$$

3 Marks

- e. Simplify the Boolean expression  $F = C(B + C)(A + B + C)$ .

- f. Simplify the following expression into sum of products using Karnaugh map  $F(A,B,C,D)$

$$= \sum (1, 3, 4, 5, 6, 7, 9, 12, 13)$$

7 Marks

### QUESTION TWO 20 MARKS

- a. By use of the postulates learnt in class, prove the following: i.  $x + x = x$  and ii.  $x \cdot x = x$

5 Marks

- b. Express the Boolean function  $F = xy + x'z$  as a product of maxterms.

6 Marks

- c. Simplify the Boolean function

$$F(x, y, z) = \sum (0, 1, 4, 5, 6, 7)$$

5 Marks

- d. Implement the following Boolean function with NAND gates:  $F(x, y, z) = \sum (1, 2, 3, 4, 5, 7)$

4 Marks

### QUESTION THREE 20 MARKS

- a. Use K-map to find the minimum-cost SOP expression for the function

4 Marks

- b. Write the expression for Boolean function  $F(A, B, C) = \sum m(1, 4, 5, 6, 7)$  in standard POS form.

4 Marks

- c. Implement the following function using a 3 line to 8 line decoder.

4 Marks

$$S(A, B, C) = \sum m(1, 2, 4, 7)$$

$$C(A, B, C) = \sum m(3, 5, 6, 7)$$

- d. What are universal gates? Construct a logic circuit using NAND gates only for the expression  $X = A.(B + C)$ .

5 Marks

- e. Compare and contrast combinational and sequential digital circuits

3 Marks

### QUESTION FOUR 20 MARKS



- a. With relevant logic diagram and truth table explain the working of a two input EX-OR gate. 7 Marks
- b. With relevant diagram explain the working of master-slave JK flip flop. 8 Marks
- c. State and prove Demorgan's laws. 5 Marks

### QUESTION FIVE 20 MARKS

- a. What is a flip-flop? State the difference between a latch and a flip-flop and list out the applications of flip-flop. 4 Marks
- b. Implement  $f_1(X_2; X_1) = \sum m(0; 3)$ ;  $f_2(X_2; X_1) = \overline{x_2 + x_1}$ ;  $f_3(X_2; X_1) = \pi M(1)$  with a 4 x 3 ROM 9 Marks
- c. With the help of a truth table explain the working of a half Subtractor. Draw the logic diagram using gates. 7 Marks