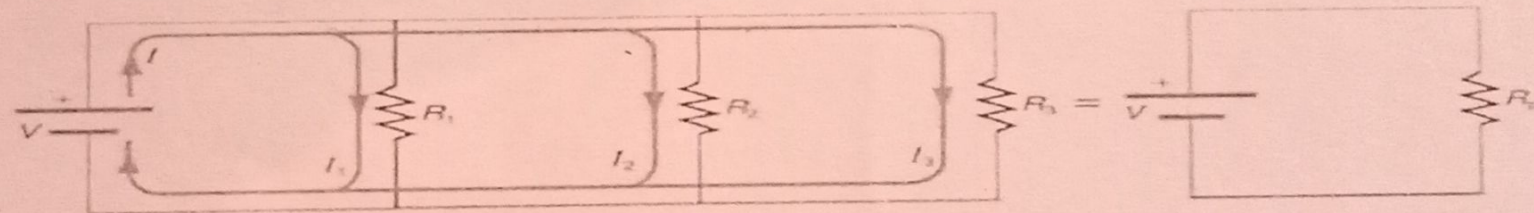


1. A series RLC resonant circuit has a resonant frequency admittance of 2×10^{-2} S(mohs). The Q of the circuit is 50, and the resonant frequency is 10,000 rad/sec. Calculate the values of R, L, and C. (7 Marks)
2. Given a 10 Vrms and 50 Hz power source hooked up in series to a 0.04 H inductor, a 5Ω resistor, and 0.01 F capacitor. Calculate the impedance of this circuit and the resonance frequency (8 Marks)
3. From first principle prove that the effective resistance R_{eff} for three resistors (R_1 , R_2 , and R_3) connected in parallel and supplied with an emf is given by $R_{\text{eff}} = R_1 R_2 R_3 / (R_1 + R_2 + R_3)$ 6 Marks



4. The voltage applied to a series RLC circuit is 0.85V. The Q of the inductor coil is 50 and the value of the capacitor is 320 pF. The resonant frequency of the circuit is 175 KHz. Find:
 - (i) the value of inductance
 - (ii) the value of resistance
 - (iii) the voltage across capacitor
 9 Marks

