

CAT ONE 1 ¼ hours

ECE 221 : FUNDAMENTALS OF ELECTRONICS

(BASIC ELECTRONICS)

QUESTION ONE ✓

Explain the principle of operation of a center-tap rectifier using a suitable circuit and waveforms

marks

15 ✓

QUESTION TWO

Derive that the efficiency of a half wave rectifier is $\eta = \left(\frac{2}{\pi}\right)^2 \times \frac{1}{1+r+RL} \dots$

15 marks

QUESTION THREE ✓

The collector current is 9.95mA and that of a base current is 5μA.

Calculate the short-circuit current gain

15 marks

QUESTION FOUR

Describe how the dc stabilisation biasing method works using suitable circuits

15 marks

Current gain

$$\beta = \frac{I_C}{I_B}$$

$$\beta = \frac{I_C}{I_E}$$

$$\frac{I_C}{I_{C0} + I_E}$$

