

### QN1 [30mks]

- (a) i) State and explain the principle of operation of the following [4mks]  
transducers:

- Strain gauge loadcell
- Linear Potentiometer
- Eddy current sensor
- Thermocouple

- ii) Explain the following types of errors in measurements and provide ONE technique of averting the errors in each category.

- Systematic errors  $\rightarrow$  [2mks]
- random errors  $\rightarrow$  [2mks]
- Gross errors  $\rightarrow$  [2mks]

- (b) A strain gauge bonded load cell has a Young's modulus  $E = 2 \times 10^{11} \text{ N/m}^2$  and cross-section of  $15 \text{ cm}^2$ . The strain gauge of gauge factor  $G = 2.5$  and nominal resistance  $R_0 = 300 \Omega$  is aligned in the direction of tension and connected into a wheatstone bridge whose other arms have equal resistance of  $300 \Omega$ , and supply voltage  $V_s = 10 \text{ V dc}$ . If the output voltage is  $3 \text{ mV}$ , determine the following:

- Percentage change in gauge resistance due to an applied force [4mks]
- The magnitude of the applied force on the load cell [4mks]

- (c) With the aid of a well labelled circuit diagram, describe how a LVDT [6mks]  
transducer can be used to measure changes in displacement.

- (d) Consider the circuit of Fig. 1.

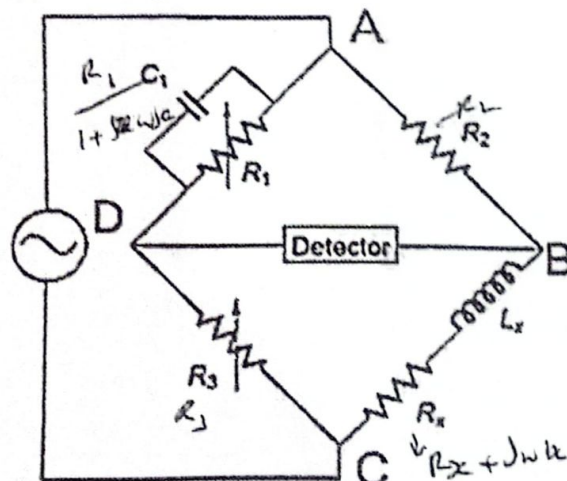


Fig. 1

$$\frac{Z_1}{Z_3} = \frac{Z_2}{Z_4}$$

$$\frac{\frac{R_1}{1+j\omega C_1}}{R_3} = \frac{R_2}{R_x + j\omega L_x}$$

$$\frac{R_1 R_3}{1+j\omega C_1} = \frac{R_2}{R_x + j\omega L_x}$$

- Derive the equations for  $R_x$  and  $L_x$  under balanced conditions [4mks]
- If the bridge parameters at balanced conditions are: [2mks]

$C_1 = 0.01 \mu\text{F}$ ,  $R_1 = 470 \text{ k}\Omega$ ,  $R_2 = 5.1 \text{ k}\Omega$ ,  $R_3 = 100 \text{ k}\Omega$ , determine the values  $R_x$  and  $L_x$ .

$$R_x = \frac{R_2 R_3}{R_1}$$

$$L_x = R_2 R_3 C_1$$

$$\frac{R_1 R_3}{R_2}$$

### QN 2 [20mks]

- (a) With the aid of a circuit diagram, explain how Eddy current sensors can detect variations in thickness of a moving aluminium sheet. [6mks]
- (b) A Piezoelectric crystal of charge sensitivity =  $2\text{pC/N}$ , area =  $1\text{cm}^2$ , thickness  $t = 0.1\text{cm}$  and  $\epsilon_r = 5$ , is subjected to a force of  $5\text{N}$ . Two metal electrodes measure changes in voltage in the crystal. Take  $E = 9 \times 10^{10}\text{Pa}$ , and  $\epsilon_0 = 8.85 \times 10^{-12}\text{F/m}$ . Calculate:  $C = \frac{Q}{V}$
- the voltage across the electrodes [3mks]
  - the change in crystal thickness [4mks]
- (c) A series circuit of Fig. 2 is connected to a  $250\text{V}$  dc source. Resistor  $R_2$  is measured by voltmeters A and B having sensitivities of  $500\Omega/\text{V}$  and  $10\text{k}\Omega/\text{V}$  respectively. If both meters are used on the  $150\text{V}$  range, determine the percentage error for each voltage measurement. [7mks]

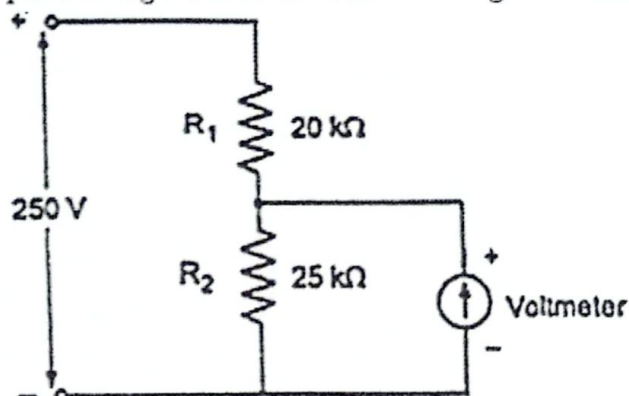


Fig. 2

$$\frac{500}{150} = 3.333\Omega$$

$$q = 5d$$

$$\frac{q}{c} = V$$

$$= 2.25$$

$$\frac{2 \times 10^{-14}}{8.85 \times 10^{-12} \times 5} \times 0.1 \times 10^{-2}$$

$$= 2.25$$

### QN 3 [20mks]

- (a) Explain how a cathode ray oscilloscope (CRO) can be used to determine the dc voltage, rms voltage, current, phase difference and frequency of an ac signal. [8mks]
- (b) State FOUR differences between dual trace and dual beam oscilloscopes. [4mks]
- (c) The Fig. 3 shows the waveforms of a dual channel CRO with vertical sensitivity and timebase settings.

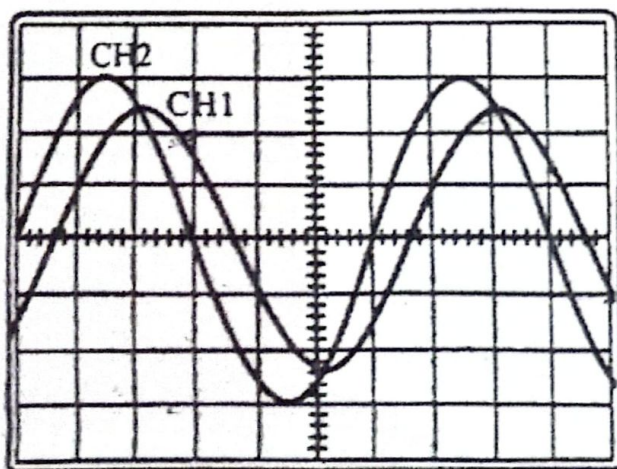


Fig. 3

Vertical sensitivity:

$$V_1: \text{CH1} = 2\text{V/div}$$

$$V_2: \text{CH2} = 5\text{V/div}$$

Timebase setting:

$$5\text{ms/div}$$

- Determine the period and frequency of  $V_1$  and  $V_2$  [2mks]
- The peak to peak value of  $V_1$  and  $V_2$  [2mks]
- The rms value of  $V_1$  and  $V_2$  [2mks]
- The phase angle of  $V_1$  relative to  $V_2$  [2mks]



#### QN 4 [20mks]

- (a) With the aid of a circuit diagram, explain how the Q-meter measures the quality factor of an unknown coil at radio frequencies. [6mks]
- (b) The bridge of Fig. 4 has the following components:  
Arm AB: Unknown inductance  $L_1$  with resistance  $R_1$   
Arm BC:  $R_2 = 200\Omega$ ; Arm CD:  $R_3 = 100\Omega$   
Bridge balance is obtained when  $L_4 = 50mH$  and  $R_4 = 2\Omega$   
i) Derive the equations for the unknown values  $L_1$ , and  $R_1$  [4mks]  
ii) Determine  $L_1$ ,  $R_1$  and Q-factor for  $f = 50\text{ Hz}$ . [3mks]

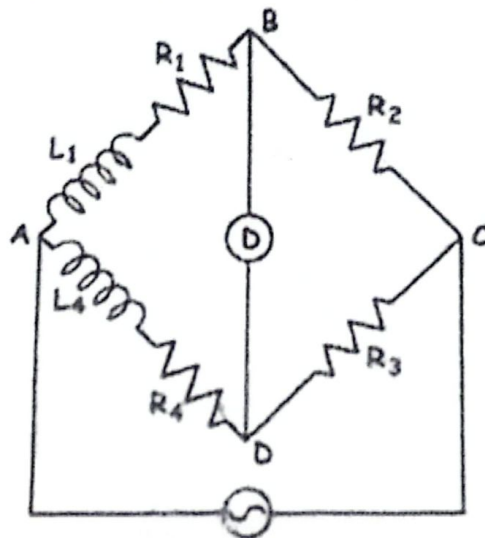


Fig. 4

- (c) With the aid of a circuit diagram, describe how digital multimeters are used in measurement of d.c. and a.c. voltages, currents and resistance. [7mks]

#### QN 5 (20mks)

- (a) i) State FIVE differences between active matrix and passive matrix displays [5mks]  
ii) Describe with the aid of diagrams how a  $5 \times 7$  dot matrix type of LED display can be used to display any three characters of the alphabet. [7mks]  
iii) Briefly explain the working principle of plasma displays [2mks]
- (b) A coil of resistance  $10\Omega$  is connected in the Q-meter circuit. Resonance occurs at a frequency of  $1\text{MHz}$  with the tuning capacitor set to  $45pF$ . Calculate the percentage error introduced in the calculated Q-value if a shunt resistance of  $0.02\Omega$  is used to stabilize the input voltage. [6mks]